

# Baugh-Wooley Multiplier

## 1 Objectives

- Understand the Baugh-Wooley multiplication algorithm for 2's complement data.
- Design a 2's complement multiplier based on the Baugh-Wooley algorithm.
- Employ hierarchical design technique.
- Simulate the multiplier performance.

## 2 Introduction

We start by explaining the Baugh-Wooley multiplication algorithm.

### 2.1 Multiplying two 2's complement numbers

The Baugh-Wooley multiplication algorithm is an efficient way to handle the sign bits. This technique has been developed in order to design regular multipliers, suited for 2's-complement numbers. Let us consider two  $n$ -bit numbers,  $A$  and  $B$ , to be multiplied.  $A$  and  $B$  can be represented as

$$A = -a_{n-1}2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i \quad (1)$$

$$B = -b_{n-1}2^{n-1} + \sum_{i=0}^{n-2} b_i 2^i \quad (2)$$

Where the  $a_i$ 's and  $b_i$ 's are the bits in  $A$  and  $B$ , respectively, and  $a_{n-1}$  and  $b_{n-1}$  are the sign bits.

The product,  $P = A \times B$ , is then given by the following equation:

$$\begin{aligned} P &= A \times B \\ &= \left( -a_{n-1}2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i \right) \times \left( -b_{n-1}2^{n-1} + \sum_{j=0}^{n-2} b_j 2^j \right) \\ &= a_{n-1}b_{n-1}2^{2n-2} + \sum_{i=0}^{n-2} \sum_{j=0}^{n-2} a_i b_j 2^{i+j} \\ &\quad - 2^{n-1} \sum_{i=0}^{n-2} a_i b_{n-1} 2^i - 2^{n-1} \sum_{j=0}^{n-2} a_{n-1} b_j 2^j \end{aligned} \quad (3)$$

Equation (3) indicates that the final product is obtained by subtracting the last two *positive terms* from the first two terms.

## 2.2 Baugh-Wooley multiplication algorithm

Rather than do a subtraction operation, we can obtain the 2's complement of the last two term and add all terms to get the final product.

The last two terms are  $n - 1$  bits each that extend in binary weight from position  $2^{n-1}$  up to  $2^{2n-3}$ . On the other hand, the final product is  $2n$  bits and extends in binary weight from  $2^0$  up to  $2^{2n-1}$ .

We pad each of the last two terms in Equation (3) with zeros to obtain a  $2n$ -bit number to be able to add them to the other terms. The padded terms extend in binary weight from  $2^0$  up to  $2^{2n-1}$ .

Assuming  $X$  is one of the last two terms we can represent it with zero padding as

$$X = -0 \times 2^{2n-1} + 0 \times 2^{2n-2} + 2^{n-1} \sum_{i=0}^{n-2} x_i 2^i + \sum_{j=0}^{n-2} 0 \times 2^j \quad (4)$$

The above equation gives the *value* of  $X$  due to the fact that a negative value is associated with the MSB.

When we *store*  $X$  in a register, the negative sign at MSB is not used since  $X$  is stored as a *binary pattern*. Thus partial product  $X$  is, therefore, represented by

|              |          |          |           |           |         |       |         |         |         |         |     |
|--------------|----------|----------|-----------|-----------|---------|-------|---------|---------|---------|---------|-----|
| bit position | $2n - 1$ | $2n - 2$ | $2n - 3$  | $2n - 4$  | $\dots$ | $n$   | $n - 1$ | $n - 2$ | $n - 3$ | $\dots$ | $0$ |
| bit value    | 0        | 0        | $x_{n-2}$ | $x_{n-3}$ | $\dots$ | $x_1$ | $x_0$   | 0       | 0       | $\dots$ | 0   |

The two's complement of  $X$  is obtained by complimenting all bits in the above equation and adding '1' at the LSB:

|              |          |          |           |           |         |       |         |         |         |         |         |
|--------------|----------|----------|-----------|-----------|---------|-------|---------|---------|---------|---------|---------|
| bit position | $2n - 1$ | $2n - 2$ | $2n - 3$  | $2n - 4$  | $\dots$ | $n$   | $n - 1$ | $n - 2$ | $n - 3$ | $\dots$ | $0$     |
| bit value    | 1        | 1        | $x_{n-2}$ | $x_{n-3}$ | $\dots$ | $x_1$ | $x_0$   | 1       | 1       | $\dots$ | $1 + 1$ |

Adding the '1' at LSB will result in the new pattern for  $-X$  as

|              |          |          |           |           |         |       |           |         |         |         |     |
|--------------|----------|----------|-----------|-----------|---------|-------|-----------|---------|---------|---------|-----|
| bit position | $2n - 1$ | $2n - 2$ | $2n - 3$  | $2n - 4$  | $\dots$ | $n$   | $n - 1$   | $n - 2$ | $n - 3$ | $\dots$ | $0$ |
| bit value    | 1        | 1        | $x_{n-2}$ | $x_{n-3}$ | $\dots$ | $x_1$ | $x_0 + 1$ | 0       | 0       | $\dots$ | 0   |

Assuming the last two terms are expressed as  $X$  and  $Y$ , then adding  $-X$  to  $-Y$  amounts to adding the following two bit patterns:



 


Figure 1: Block diagram of  $4 \times 4$  Baugh-Wooley multiplier



(a) Baugh-Wooley multiplier white-cell

(b) Baugh-Wooley multiplier gray-cell

Figure 2: Baugh-Wooley multiplier basic cell construction

### 3 Pre-Lab Report

1. Estimate the delay of the  $4 \times 4$  Baugh-Wolley multiplier. The gate delays are listed in Table 1.
2. Draw a block diagram of an  $8 \times 8$  Baugh-Wooley multiplier.

Table 1: CMOS gate delays and areas normalized relative to an inverter.

| Gate           | Delay | Area       | Comment   |
|----------------|-------|------------|---|
| Inverter       | 1     | 1          | Minimum delay   |
| 2-input NOR    | 1     | 3          | More area to produce delay equal to that of an inverter |
| 2-input NAND   | 1     | 3          | More area to produce delay equal to that of an inverter |
| 2-input AND    | 2     | 4          | Composed of NAND followed by inverter                   |
| 2-input OR     | 2     | 4          | Composed of NOR followed by inverter                    |
| 2-input XOR    | 3     | 11         | Built using inverters and NAND gates                    |
| $n$ -input OR  | 2     | $n/3 + 2$  | Uses saturated load                                     |
| $n$ -input AND | 3     | $4n/3 + 2$ | Uses $n$ -input OR preceded by inverters                |

### 4 Project Requirements

In this project you are required to design, model, and simulate a  $4 \times 4$  multiplier based on the Baugh-Wooley algorithm.

1. The  $4 \times 4$  Baugh-Wooley multiplier is to be hierarchically designed using 1-bit full adders and the two types of cells shown in Figure 1.
2. The delays of the components should be assigned with the help of Table 1 and assuming the delay of an inverter is 1 ns.
3. The multiplier has two inputs  $a$  and  $b$  of type **signed** representing the multiplier and multiplicand; and one output  $p$  of type **signed** representing the product.
4. Write a testbench to verify the operation of the multiplier. The testbench should try different number values and signs. Simulate the behavior of the multiplier using the testbench you developed.

## 5 Lab Report

1. Refer to the lab report grading scheme for items that must be present in your report.
2. Estimate the area of a  $4 \times 4$  Baugh-Wolley multipliers. The gate areas are listed in Table 1.
3. Find the delay of the  $4 \times 4$  multiplier using the waveform you got from simulation and comment on your results.