

## LINEAR TIME INVARIANT SYSTEMS


- output is a LINEAR function of the input
- can be represented by LINEAR differential equations
  - no product terms
  - no power terms
  - no time-varying parameters

$$A\ddot{y}(t) + B\dot{y}(t) + Cy(t) = x(t)$$

- obey the principle of superposition

# Analogous Systems

Electrical

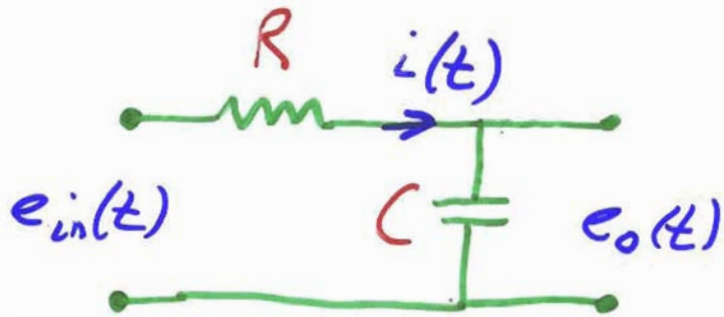

$$e_{in}(t) = R i(t) + \frac{1}{C} \int i(t) dt$$

$$i(t) = \dot{q}(t)$$

$$e_o(t) = \frac{1}{C} q(t)$$


$$e_{in}(t) = R \dot{q}(t) + \frac{1}{C} q(t)$$

$$i(t) = C \dot{e}_o(t)$$

$$e_{in}(t) = RC \dot{e}_o(t) + e_o(t)$$

$$\dot{e}_o(t) + \frac{1}{RC} e_o(t) = \frac{1}{RC} e_{in}(t)$$

Mechanical

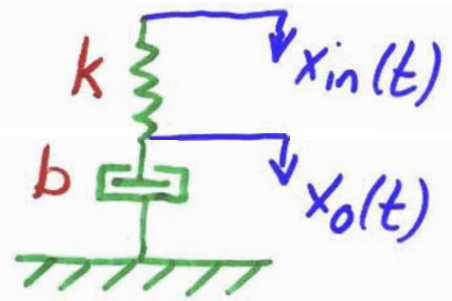

$$k(x_{in}(t) - x_o(t)) = b \dot{x}_o(t)$$


$$b \dot{x}_o(t) + k x_o(t) = k x_{in}(t)$$

$$\dot{x}_o(t) + \frac{k}{b} x_o(t) = \frac{k}{b} x_{in}(t)$$

System dynamics are identical if

$$R = b \quad \frac{1}{C} = k$$


# Second Order Systems

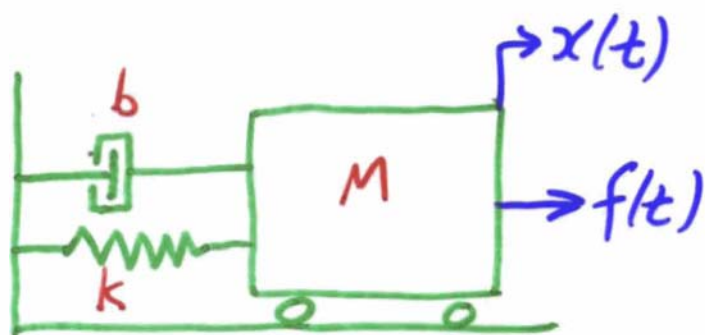

$$F = Ma$$

$$f(t) - b\dot{x}(t) - kx(t) = M\ddot{x}(t)$$
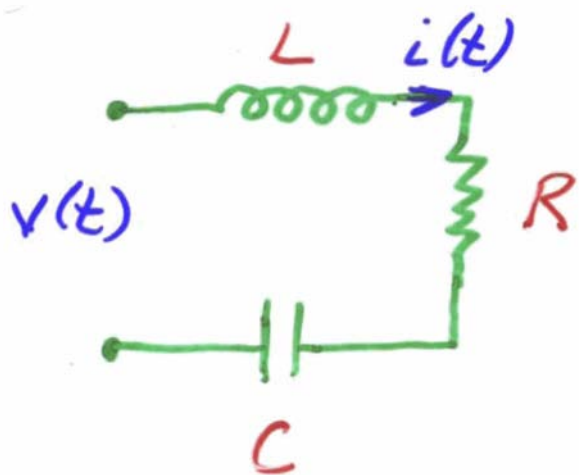
$$M\ddot{x}(t) + b\dot{x}(t) + kx(t) = f(t)$$



$$L\dot{i}(t) + Ri(t) + \frac{1}{C} \int i(t) dt = v(t)$$


$$L\ddot{q}(t) + R\dot{q}(t) + \frac{1}{C} q(t) = v(t)$$

**TABLE 4-1** FORCE-VOLTAGE ANALOGY

Mechanical systems	Electrical systems
<p>Force <math>p</math> (torque <math>T</math>)</p> <p>Mass <math>m</math> (moment of inertia <math>J</math>)</p> <p>Viscous-friction coefficient <math>b</math></p> <p>Spring constant <math>k</math></p> <p>Displacement <math>x</math> (angular displacement <math>\theta</math>)</p> <p>Velocity <math>\dot{x}</math> (angular velocity <math>\dot{\theta}</math>)</p>	<p>Voltage <math>e</math></p> <p>Inductance <math>L</math></p> <p>Resistance <math>R</math></p> <p>Reciprocal of capacitance, <math>1/C</math></p> <p>Charge <math>q</math></p> <p>Current <math>i</math></p>

# Inertial Elements

Diagram

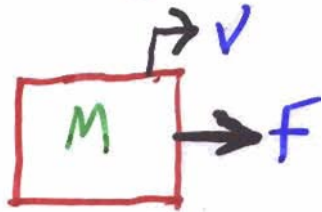


state variable

$v$ , velocity


equation
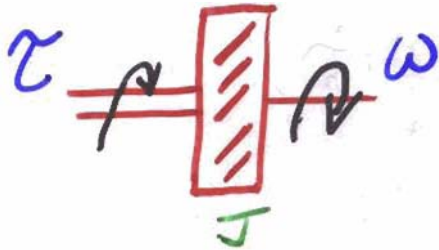
$$M\dot{v} = F$$
$$\dot{v} = \frac{1}{M} F$$



$\omega$ , angular velocity

$$J\dot{\omega} = \tau$$

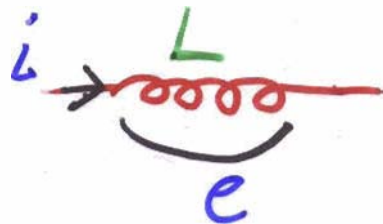


$i$ , current  $L\dot{i} = e$

All store Energy

# Capacitive Elements

Diagram

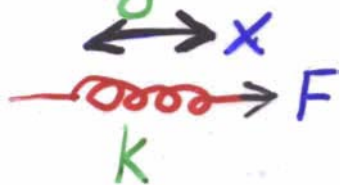

state variable

$x$ , compression  
or extension  
( $\Delta x$ )


equation

$$F = kx$$



$\theta$  twist  
( $\Delta \theta$ )

$$T = k\theta$$

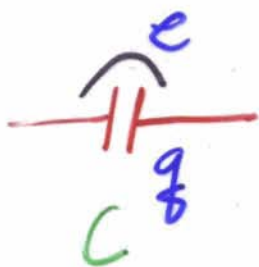

$q$ , charge on C


$$e = \frac{1}{C} q$$

$$e = \frac{1}{C} \int i(t) dt$$

All store Energy

# Dissipative Elements


Diagram

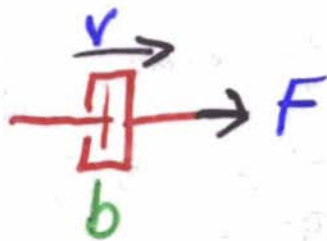

equation


$$F = bv = b\dot{x}$$

$$T = b\dot{\theta} = b\dot{\omega}$$

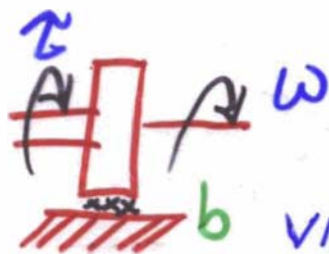

$$T = b\omega$$

viscous (bearing)  
friction

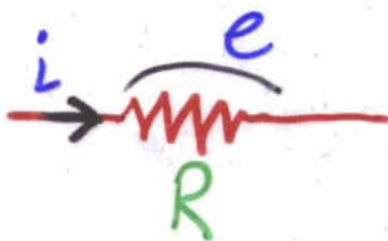


$$e = Ri$$

$$v = Ri$$

All dissipate Energy (heat)

# Transformer Elements

Diagram

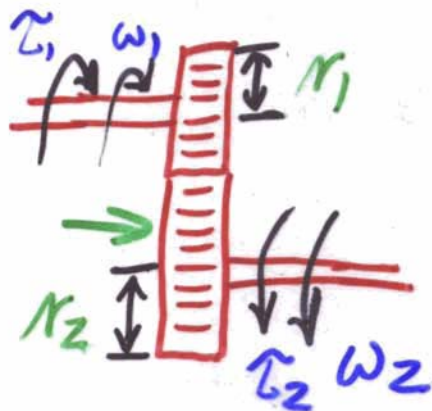



equation

$$\tau_2 = \frac{n_2}{n_1} \tau_1, \quad \omega_2 = \frac{n_1}{n_2} \omega_1$$

$$\tau_1 \omega_1 = \tau_2 \omega_2$$

$$V_2 = \frac{n_2}{n_1} V_1, \quad I_2 = \frac{n_1}{n_2} I_1$$

$$V_1 I_1 = V_2 I_2$$

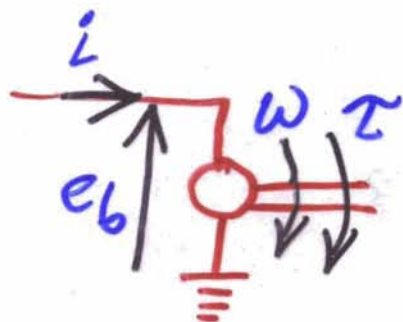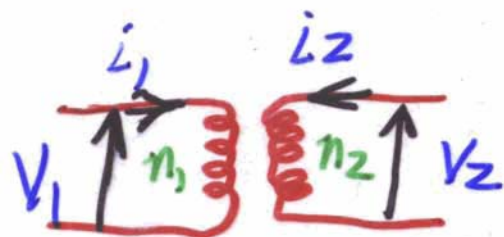


$$\tau = k_t i, \quad e_b = k_t \omega$$

$$e_b i = \tau \omega$$

These devices neither store nor dissipate energy

# Example 1

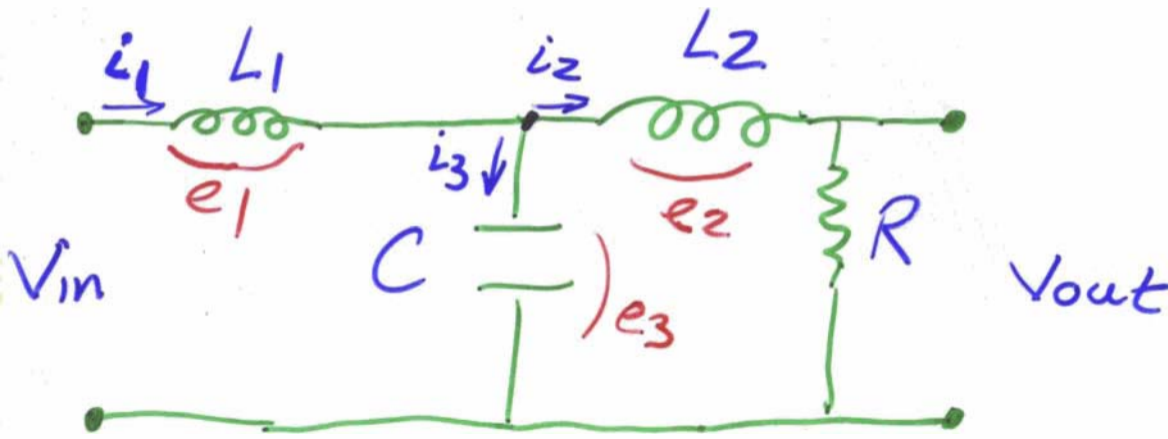

KVL loop 1

$$V_{in} = \dot{i}_1 L_1 + q/c \Rightarrow \dot{i}_1 = \frac{-q}{L_1 C} + \frac{V_{in}}{L_1}$$

node currents

$$i_1 = i_2 + i_3 \Rightarrow i_3 = i_1 - i_2 \Rightarrow \dot{q} = L_1 \dot{i}_1 - L_2 \dot{i}_2$$

KVL loop 2

$$L_2 \dot{i}_2 + i_2 R - q/c = 0 \Rightarrow \dot{i}_2 = \frac{q}{L_2 C} - \frac{i_2 R}{L_2}$$

In matrix form

$$\begin{bmatrix} i_1 \\ q \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & -1/L_1 C & 0 \\ 1 & 0 & -1 \\ 0 & 1/L_2 C & -R/L_2 \end{bmatrix} \begin{bmatrix} i_1 \\ q \\ i_2 \end{bmatrix} + \begin{bmatrix} 1/L_1 \\ 0 \\ 0 \end{bmatrix} V_{in}$$

$\times$   $A$   $\times$   $B$   $u$

$$V_{out} = \begin{bmatrix} 0 & 0 & R \end{bmatrix} \begin{bmatrix} i_1 \\ q \\ i_2 \end{bmatrix}$$

$y$   $C$   $\times$

Alternate form

$$\begin{bmatrix} \dot{V}_0 \\ \ddot{V}_0 \\ \ddot{V}_0 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ \frac{-R}{L_1 L_2 C} & \frac{-(L_1 + L_2)}{L_1 L_2 C} & -\frac{R}{L_2} \end{bmatrix} \begin{bmatrix} V_0 \\ \dot{V}_0 \\ \ddot{V}_0 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ \frac{R}{L_1 L_2 C} \end{bmatrix}$$

$$V_0 = \begin{bmatrix} 1 & 0 & 0 \end{bmatrix} \cdot \begin{bmatrix} V_0 \\ \dot{V}_0 \\ \ddot{V}_0 \end{bmatrix}$$